

EE446 PRELIMINARY WORK #3**Laboratory Work 3 - Single Cycle Processor Design*****Introduction:***

The goal of this laboratory exercise is to practice designing a 32-bit single cycle processor. I will build a single cycle processor datapath and control unit similar to the one covered in class. The developed processor will be able to carry out all of the instructions in the instruction set.

During this laboratory work, I will improve your hard-wired controller design skills by designing the single-cycle processor's controller unit. Finally, I will test my design by embedding it in the FPGA of the -DE0-Nano board.

Preliminary Work:

Single-cycle: Each instruction executes in a single cycle

- One instruction at a time
- Separate instruction, data memories (Harvard)
- Simple control, no need for non-architectural state
- Cycle time is limited by the slowest instruction

The datapath:

- operates on words of data
- Contains memories, registers, ALUs, and multiplexers.
- 32-bit ARM architecture has a 32-bit datapath.

The control unit.

- receives the current instruction from the datapath
- control the operation of the datapath tells the datapath to execute that instruction.
- produces multiplexer select, register enable, and memory write signals

Combinational Read: If the address changes, then the new data appears at RD after some propagation delay; no clock is involved.

Synchronous Write: only on the rising edge of the clock.

The state of the system is changed only at the clock edge.

The address, data, and write enable must setup before the clock edge and must remain stable until a hold time after the clock edge.

The instruction memory :

- has a single read port.
- Input (A): 32-bit instruction address input from PC
- Output (RD): 32-bit data (i.e., instruction) from that address

The data memory:

- has a single read/write port.
- 32 bit address, 32 bit data word
- If write enable, (WE)=1 → writes data WD into address A on the rising edge of the clock.
- If WE=0 → reads address A onto RD

Register File (RF):

- 15-element × 32-bit Registers: R0–R14

– Read ports:

- A1 and A2: 4-bit address inputs, specifying one of 24 = 16 registers as source operands.
- RD1 and RD2: read data outputs, read the 32-bit register

– The write port:

- A3: 4-bit address input
- WD3: 32-bit write data input
- WE3: a write enable input

– If WE3=1 → then the register file writes the data into the specified register on the rising edge of the clock.

- Input port R15:

– The data presented on the INPUT port R15 is the value of the register R15 and not the actual register R15 in the register file

– When A1/A2=15 RD1/RD2 are connected to input R15 but not the internal register R15

– PC + 8 is read from RD1/RD2

– Reading R15 returns PC+8 is because of the three-stage pipeline, so the PC value read by an instruction is two instructions (or eight bytes) ahead

- Writes to R15 must be specially handled. Many instructions restrict R15 to be the destination register.

• When an instruction writes R15 the value written to R15 is treated as an instruction address and a branch occurs to that address

• PC: The address of the current instruction is kept in a 32-bit register called the program counter (PC), which is register R15.

- PC is an alternative name for R15

– logically part of the register file

– read and written on every cycle independent of the normal register file operation → RF read/write ports are not used


– more naturally built as a stand-alone 32-bit register.

– Output (PC): address of current instruction

– Input (PC'): address of the next instruction

STR Immediate instruction: $STR\ R_d, [R_n, imm12]$

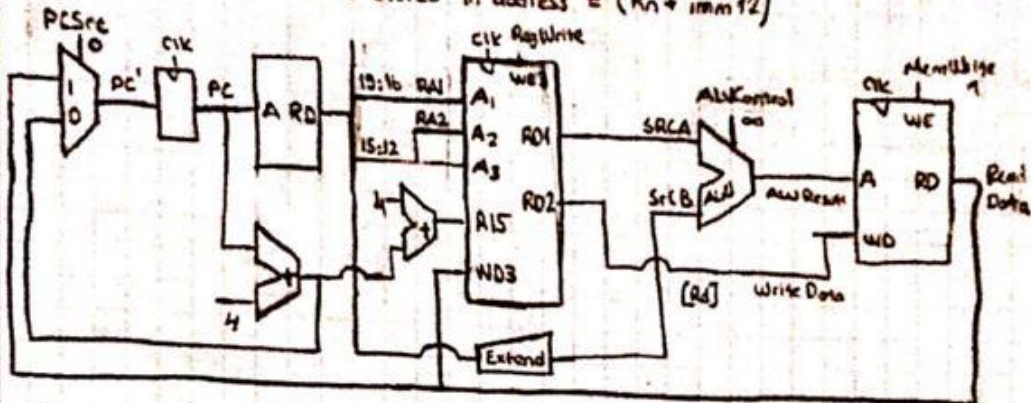The content of R_d is stored in address = $(R_n + imm12)$




Address computation is already implemented.

Reads R_d from the memory by also connecting it to the read port A2 [R_d] is on $RD2$.

[R_d] is written in the Data Memory at address $ExtImm + [R_n]$

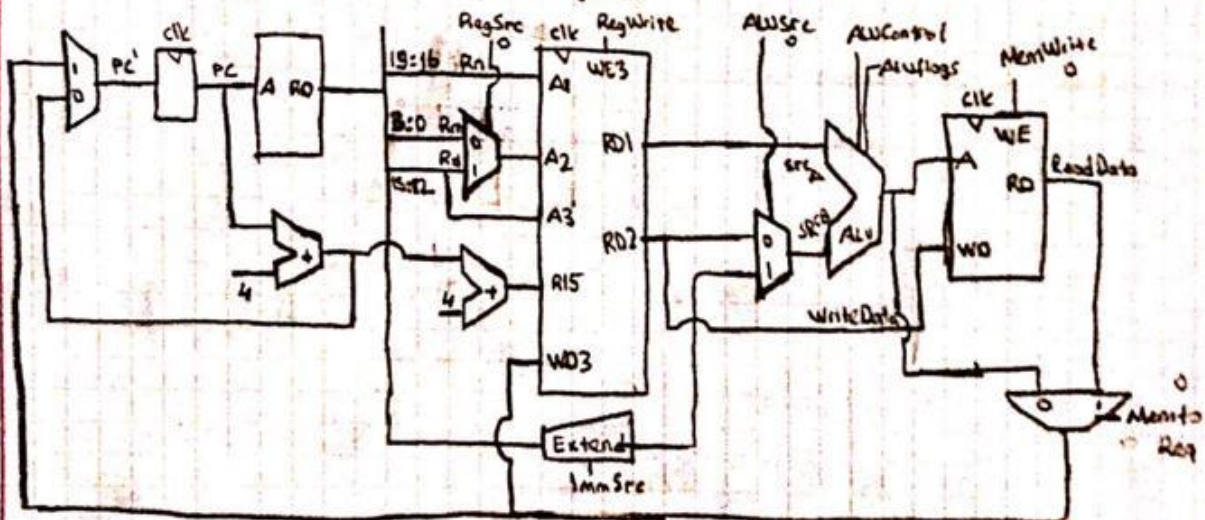$RegWrite=0$, $MemWrite=1$, Read Data is ignored.



Expand datapath to handle Data-processing. Data processing instructions \rightarrow ADD-SUB-OR-AND

Read a source register R_n from the register file and Operand.

Perform some ALU operation on them, Write the result back R_d register.

ALU control signals select which operation to be executed.

ALU flags (3:0) \rightarrow Zero, Negative, Carry, Overflow, that are sent back to the controller.

$RegSrc=0 \rightarrow RA2=R_n$ (Data Processing), $RegSrc=1 \rightarrow RA2=R_d$ (STR)

$ImmSrc=0 \rightarrow ExtImm$ is zero extended from Instr (7:0)

$ImmSrc=1 \rightarrow ExtImm$ is zero extended from Instr (11:0) for LDR or STR

$ALUSrc=0 \rightarrow SrcB=[R_n]$, $ALUSrc=1 \rightarrow SrcB=ExtImm:imm8$

$MemtoReg=0 \rightarrow Result=ALUResult$, $MemtoReg=1 \rightarrow Result=ReadData$

A combinational shifter is added to the $RD1$ output of the RF.

$RD1$ output and shifter output are mixed together and connected to the $SrcA$ input of ALU.

Shifter has 2 inputs. One of them is the output of $RD1$, the other one is $ExtImm$.

Shifts determine the shift amount

$SrcB$ input of the ALU changed with 4:1 MUX. '0' is connected to this as a 3. input.


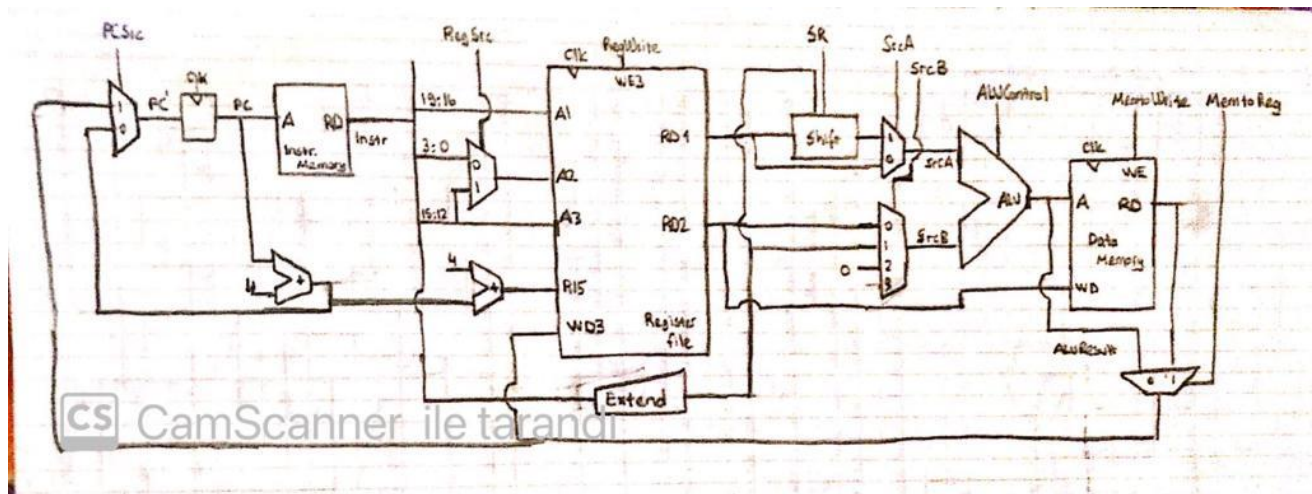


Figure 1. Overall Datapath

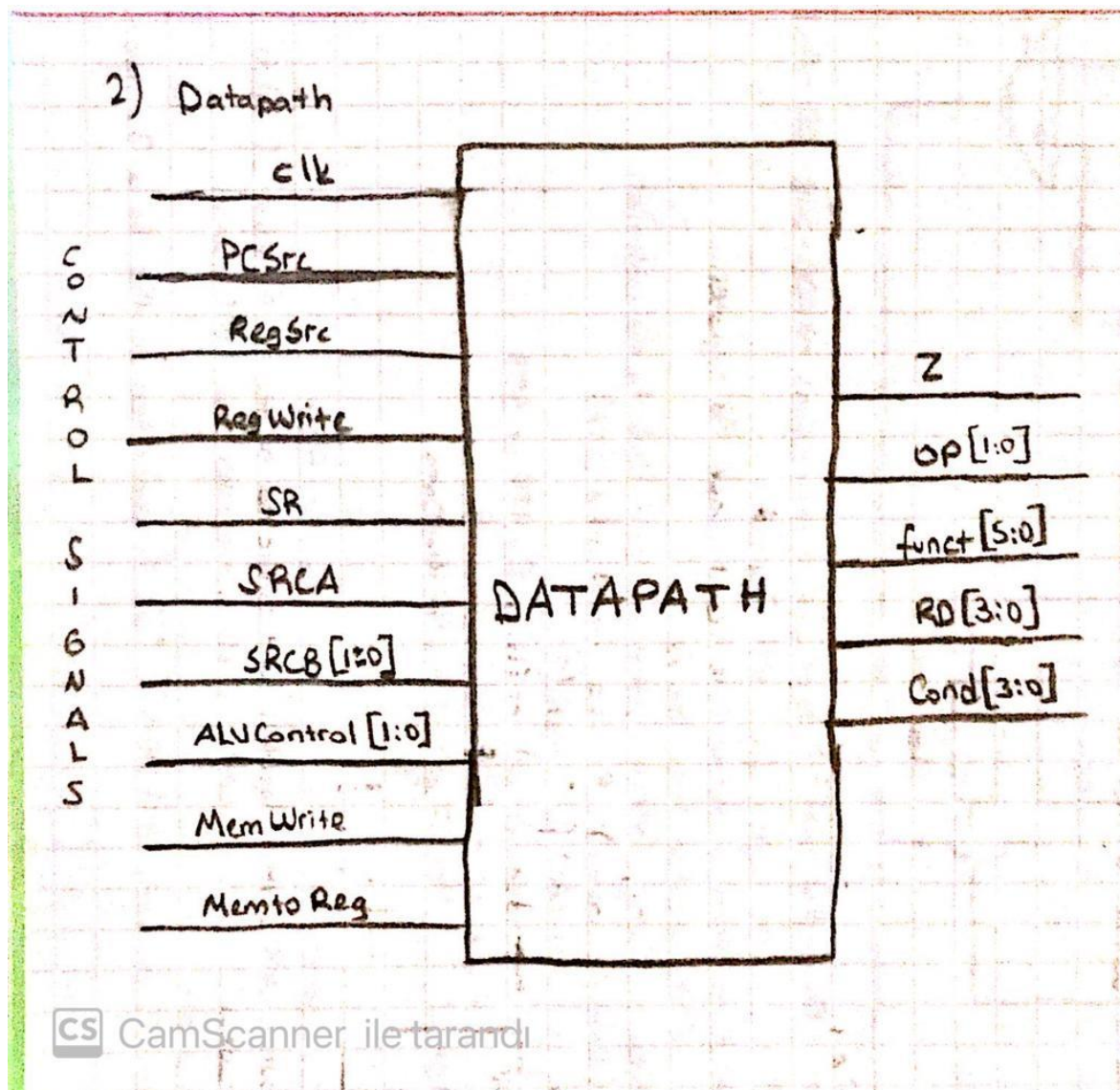2. I state the control signal inputs of my overall design in previous part. Now, I draw a black box diagram of my architecture by indicating the inputs and outputs.



The diagram illustrates a 16-bit ALU architecture with various functional units and control signals. The components and their parameters are as follows:

- Control Signals (Inputs):**
 - MUX A2 source
 - MEMDATA memdata
 - OR
 - MUX MUX source
 - OR
 - OP mem mem
 - OP mem mem
 - OP mem mem
 - MUX ALU source
 - MUX PC source
 - SHIFT left
 - MUX ALU source
- Functional Units and Parameters:**
 - ADD (Addition):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - SUB (Subtraction):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - SHL (Shift Left):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - SHR (Shift Right):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - ROL (Rotate Left):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - ROR (Rotate Right):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - ROLW (Rotate Left Word):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - RORW (Rotate Right Word):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - ROLV (Rotate Left Vector):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - RORV (Rotate Right Vector):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - ROLW1 (Rotate Left Word 1):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - RORW1 (Rotate Right Word 1):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - ROLV1 (Rotate Left Vector 1):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.
 - RORV1 (Rotate Right Vector 1):** Parameters: A1, A2, B1, B2, C1, C2, D1, D2, E1, E2, F1, F2, G1, G2, H1, H2, I1, I2, J1, J2, K1, K2, L1, L2, M1, M2, N1, N2, O1, O2, P1, P2, Q1, Q2, R1, R2, S1, S2, T1, T2, U1, U2, V1, V2, W1, W2, X1, X2, Y1, Y2, Z1, Z2.


Figure 2. Implementation of my datapath design in Schematic Editor of Quartus

1.2.2 Controller Design:

1.2.

Controller:

1)

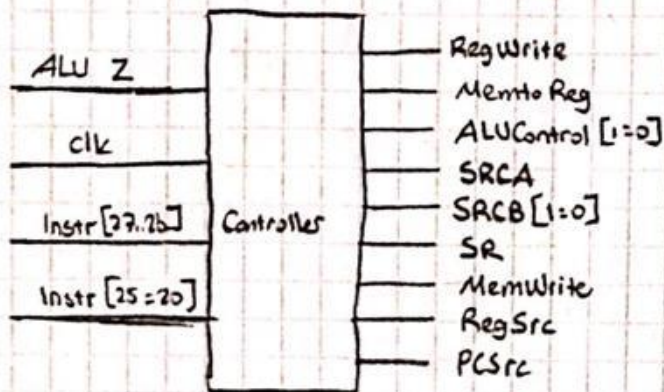

2)

We don't need to access to memory in the ADD, SUB, OR, AND instructions. The only difference btw. them is the ALUControl signal.

PC has a mux at its inputs

This MUX has a select (PCSrc).

ALU result is muxed with Read Data.

This MUX has a select (MemtoReg)

When we consider LSL, LSR instructions, we understand SR signal is necessary. SR signal of the shifter is handled by controller.

For CMP, the write enable of Z register to 1,

For STR, 2x1 Mux is added to the A2 input of the RF.

It has a select signal called RegSrc

Memwrite is added.

For LDR, RegWrite is added.

2x1 Mux is added to SRCA input of the ALU.

It has a select signal called SRCA.

It selects RD1 or output of shifter.

4x1 Mux is added to SRCB input of the ALU.

It has a select signal called SrcB.

It selects RD2 or ExtImm or 0.

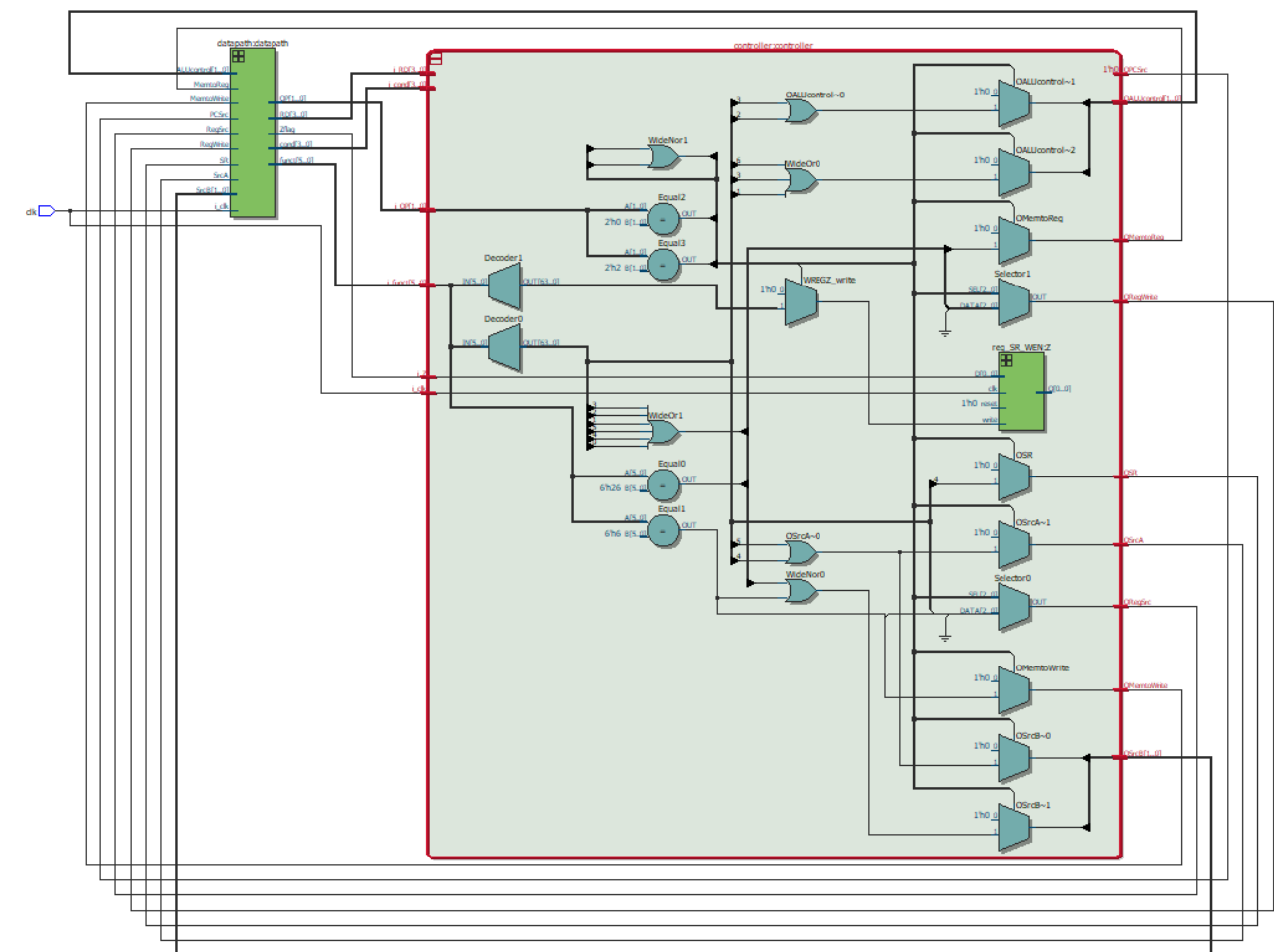
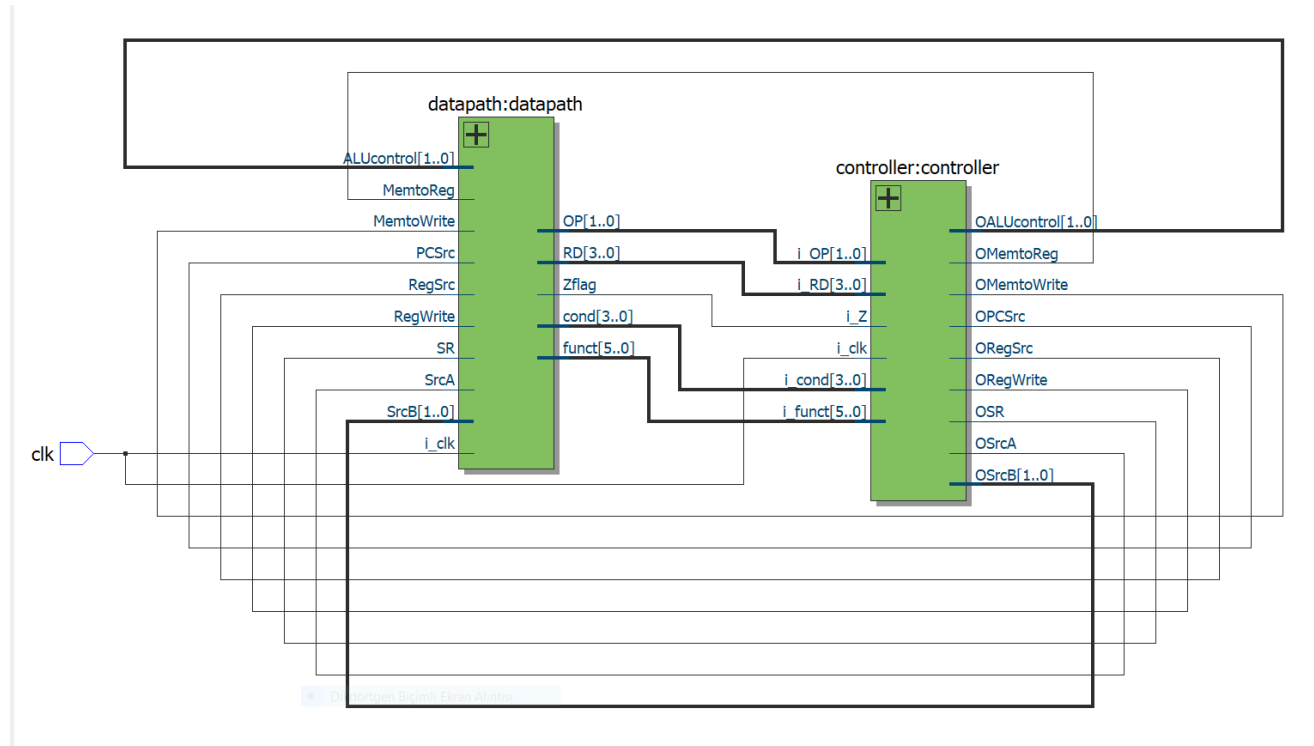


Figure 3. RTL Viewer of the controller

3.

3)	RegSrc	PCSrc	SrcA	SrcB	SR	ALUControl	RegWrite	MemWrite	MemtoReg
ADD	0	0	0	00	x	00	1	0	0
SUB	0	0	0	00	x	01	1	0	0
AND	0	0	0	00	x	10	1	0	0
OR	0	0	0	00	x	11	1	0	0
LSR	0	0	1	10	1	00	1	0	0
LSL	0	0	1	10	0	00	1	0	0
CMP	1	0	0	00	x	01	0	0	0
STR	1	0	0	01	x	0x	0	1	0
LDR	0	0	0	01	x	0x	1	0	1

Figure 4. The truth table for the main controller of the single-cycle processor

4.

I implemented my controller in Verilog HDL. It is uploaded to ODTUCLASS.

Simulation Results: I will show a simulation of the instructions below.

```
//LDR R1,[R6,#0]      R1 = 6
//LDR R2, [R6,#4]      R2 = 2
//ADD R3,R2,R1         R3 = 8
//SUB R4,R1,R2         R4 = 4
//LSL R5,R4,#1         R5 = 8
//CMP R5,R3            Z_Reg = 1
//CMP R5,R2            Z_Reg = 0
//STR R5,[R5,#8]       memory 16 -> 08
//LDR R7,[R6,#24]      R7 = FF00FF00
//LDR R8,[R6,#28]      R8 = 00FFFF00
//AND R9,R8,R7         R9 = 0000FF00
//ORR R10,R8,R7        R10 = FFFFFFF00
//LSR R11,R9,#8        R11 = 000000FF
```

 


Figure 5. Simulation showing register values and z flag.

 


Figure 6. Memory

Initially, all register values are 0.

1. Clock cycle: **LDR R1,[R6,#0]** → **R1 = 6** since memory location 0. is 6 as you can see from Figure 4
2. Clock cycle: **LDR R2, [R6,#4]** → **R2 = 2** since memory location 4. is 2 as you can see from Figure 4
3. Clock cycle: **ADD R3,R2,R1** → **R3 = 8** since 6+2 is 8 as you can see from Figure 4.
4. Clock cycle: **SUB R4,R1,R2** → **R4 = 4** since 6-2 is 4 as you can see from Figure 4.
5. Clock cycle: **LSL R5,R4,#1** → **R5 = 8** since 4*2 is 8 as you can see from Figure 4.
6. Clock cycle: **CMP R5,R3** → **Z = 1** since 8-8 is 0 as you can see from Figure 4.
7. Clock cycle: **CMP R5,R2** → **Z = 0** since 8-2 is not 0 as you can see from Figure 4.
8. Clock cycle: **STR R5,[R5,#8]** → memory location 16. is 08 as you can see from Figure 5.
9. Clock cycle: **LDR R7,[R6,#24]** → **R7 = FF00FF00** since memory location 27.26.25.24 is FF00FF00 as you can see from Figure 5.
10. Clock cycle: **LDR R8,[R6,#28]** → **R8 = 00FFFF00** since memory location 27.26.25.24 is FF00FF00 as you can see from Figure 5.
11. Clock cycle: **AND R9,R8,R7** → **R9 = 0000FF00** as you can see from Figure 4.
12. Clock cycle: **OR R10,R8,R7** → **R10 = FFFFFFF0** as you can see from Figure 4.
13. **LSR R11,R9,#8** → **R11 = 000000FF** as you can see from Figure 4.